

Assigment-3

by:

**Vraj Desai
(110118396)**

The controller:

The design of this controller was divided into five sections.

1: The register file:

First, the R0-R7 register transfer was designed in "reg_file.vhd".

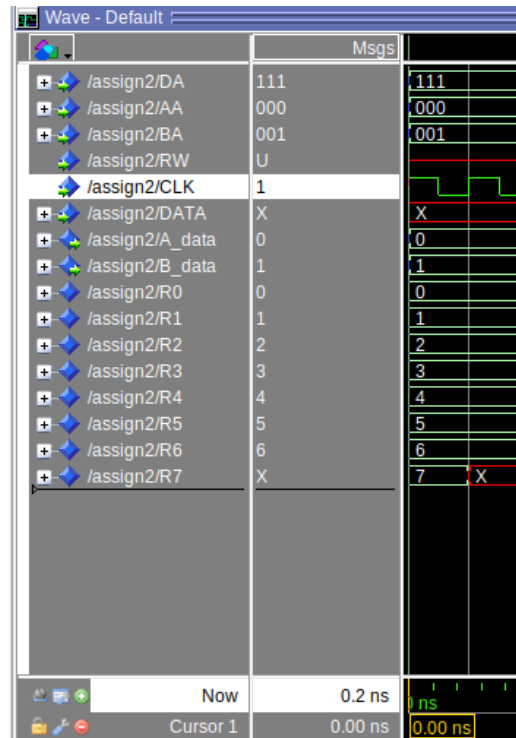


Figure 1: Register transfer file.

As seen from Fig. 1, the 0, 1 data provided with address AA and BA is transferred to R0 and R1. And at the next clock, the edge X is transferred to R7 due to DA.

2: Function Unit:

This is implemented in "fun_file.vhd".

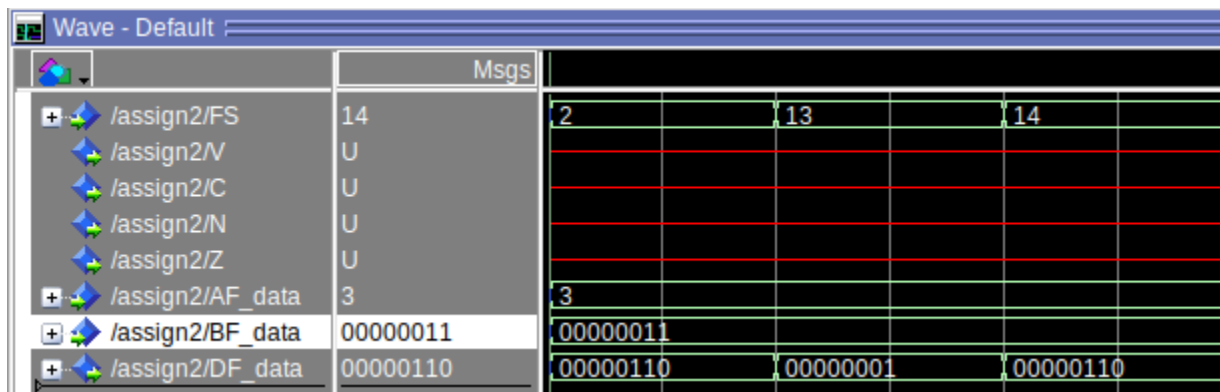


Figure 2: Function Unit

As seen from Fig. 1, the 0, 1 data provided with address AA and BA is transferred to R0 and R1. And at the next clock, the edge X is transferred to R7 due to DA.

3: Datapath:

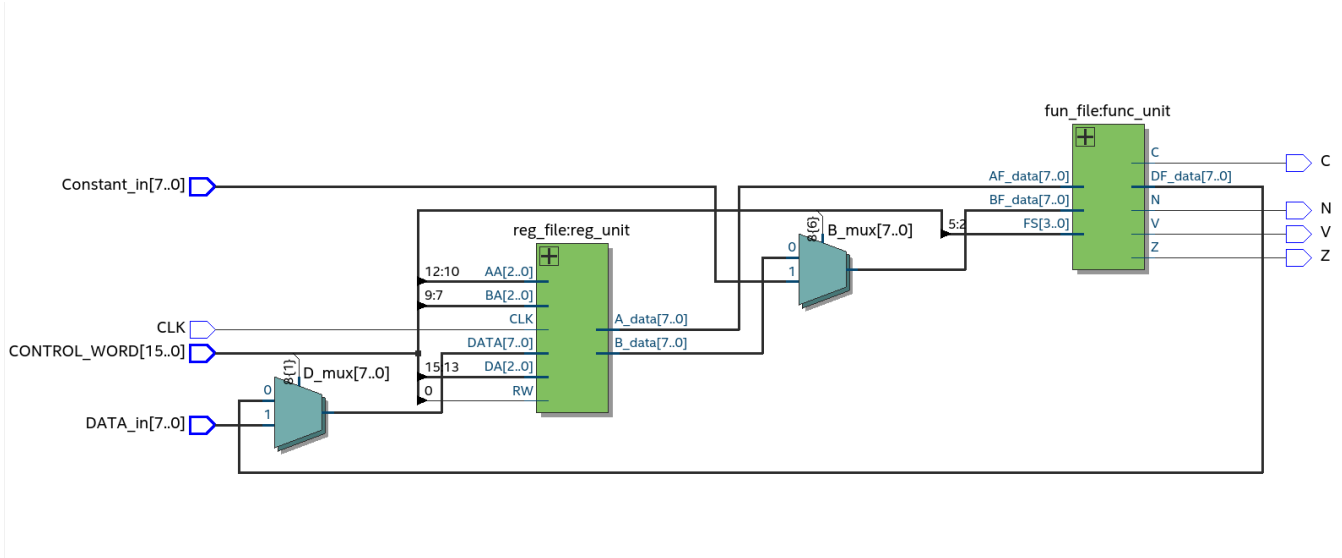


Figure 3: Datapath

The "datapath.vhd" combines "reg_file.vhd" and "fun_file.vhd" together with mux at input driven by the control word itself. The constant is muxed with reg_file output, while data_in is muxed with function unit's output.

The data path gets the control word from the memory and then performs operation from data_in or registers from reg_file. The graph of the datapath can be seen below in Fig. 4.

 


Figure 4: Datapath operation.

4: Control and Memory:

The controller generates an address when go is 1 and provides it to the memory. When the memory gets the address, and RD is high, it provides a control word to the datapath.

5: Assign2:

This file combines all the sub-blocks, as seen in Fig. 5.

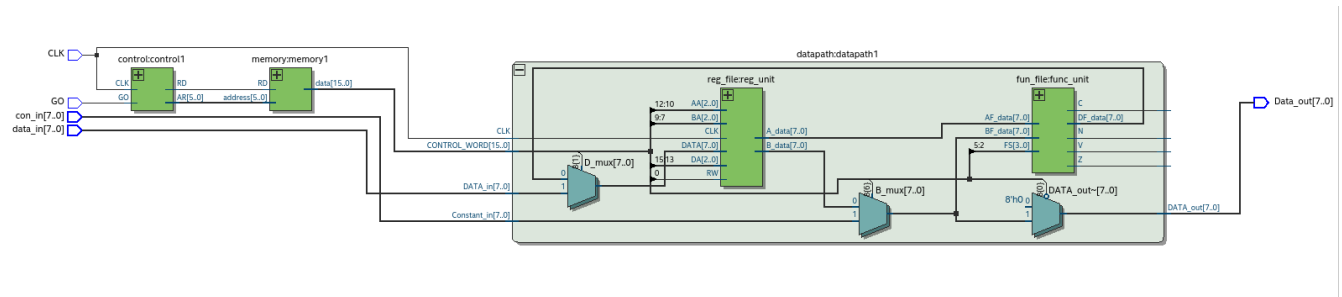


Figure 5: The controller.

As seen in Fig.5, the controller provides an address to memory, and the memory provides a control word to the datapath. And in the datapath, the sub-section reg-file and fun-file can be seen.

The final output of the controller can be seen in Fig.6 and it can be compared with fig.7 of the book.

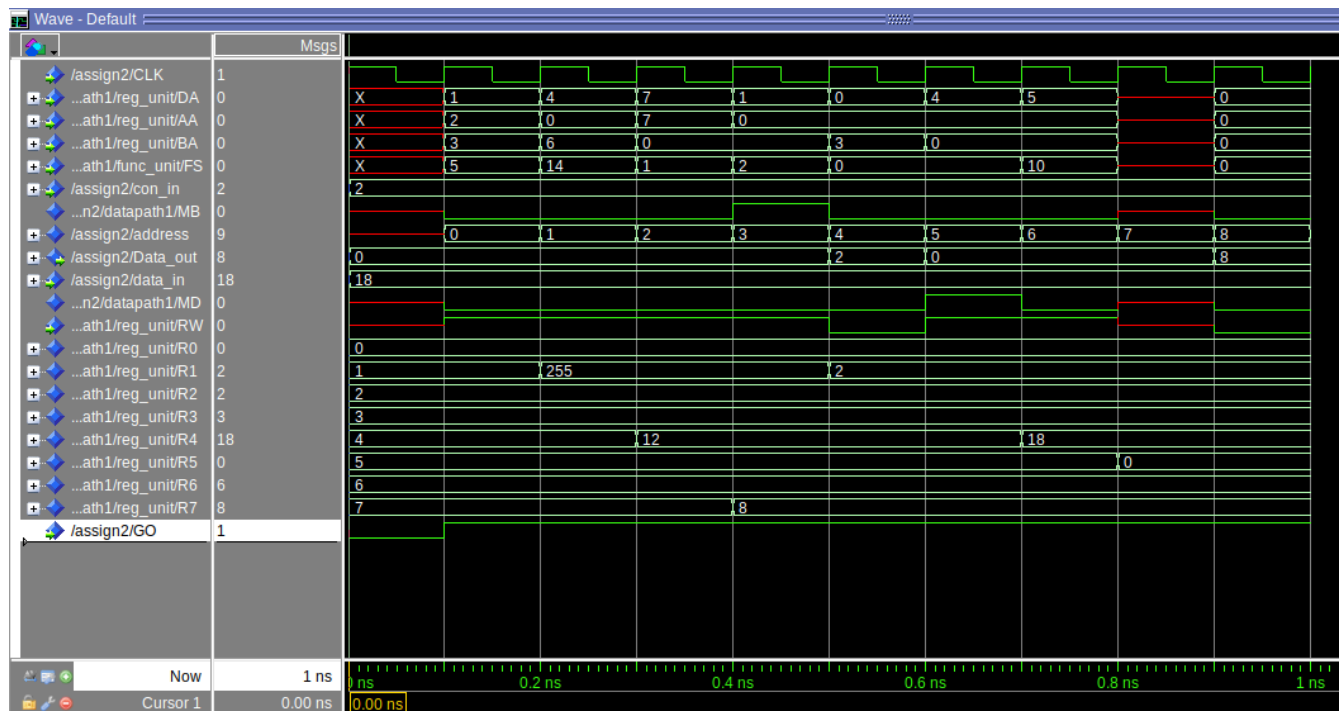


Figure 6: Controller output.

 


Figure 7: The book's controller.

Appendex:

Assign2.vhd:

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.numeric_std.all;
use ieee.std_logic_unsigned.all;

entity assign2 is
port(
    CLK, G0: in std_logic;
    Data_out: out std_logic_vector(7 downto 0);
    con_in: in std_logic_vector(7 downto 0);
    data_in: in std_logic_vector(7 downto 0)
);
end entity;

architecture BEHAVIORAL of assign2 is
component memory
port (
    address : in std_logic_vector(5 downto 0);
    data : out std_logic_vector(15 downto 0);
    RD : in std_logic
);
end component;

component control
port(
    CLK, G0: in std_logic;
    AR : out std_logic_vector(5 downto 0);
    RD : out std_logic
);
end component;

component datapath is
port(
    CONTROL_WORD: in std_logic_vector(15 downto 0);
    V, C, N, Z: out std_logic;
    CLK: in std_logic;
    Constant_in : in std_logic_vector(7 downto 0);
    DATA_in: in std_logic_vector(7 downto 0);
    DATA_out: out std_logic_vector(7 downto 0)
);
end component;

signal address: std_logic_vector(5 downto 0);
signal control_word: std_logic_vector( 15 downto 0);
```

```

signal RD_I: std_logic;
signal V,C,N,Z: std_logic;

begin

control1: control port map(CLK => CLK, GO => GO, AR => address, RD => RD_I);
memory1: memory port map(address => address, data => control_word, RD => RD_I);
datapath1: datapath port map(CONTROL_WORD => control_word, V => V, C => C, N => N,
Z => Z,
                                CLK => CLK, Constant_in =>
con_in, DATA_IN => data_in, DATA_out => Data_out);

end architecture BEHAVIORAL;

```

control.vhd:

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.numeric_std.all;
use ieee.std_logic_unsigned.all;

--Control Word ranges
-- Range DA(15:13)
-- Range AA(12:10)
-- Range BA(9:7)
-- Range MB(6)
-- Range FS(5:2)
-- Range MD(1)
-- Range RW(0)

entity control is
port(
    CLK, GO: in std_logic;
    AR : out std_logic_vector(5 downto 0);
    RD : out std_logic
);
end entity;

architecture BEHAVIORAL of control is

signal counter, counterx: std_logic_vector(5 downto 0) := B"000000";
signal RD_i : std_logic;

begin
    process(CLK, GO)
    begin
        if (rising_edge(CLK)) then
            if (GO = '1') then

```

```

        counter <= counter + 1;
    end if;
end if;
end process;
process(G0,counter)
begin
    if (G0 ='1') then
        RD_i <= '1';
        counterx <= counter;
    else
        RD_i <= '0';
        counterx <= "XXXXXX";
    end if;
end process;

RD <= RD_i;
AR <= counterx;
end architecture BEHAVIORAL;

```

memory.vdh:

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;

entity memory is
    port ( address : in std_logic_vector(5 downto 0);
          data : out std_logic_vector(15 downto 0);
          RD : in std_logic);
end entity;

architecture behavioral of memory is
    type mem is array ( 0 to 2**3 - 1) of std_logic_vector(15 downto 0);
    constant my_Rom : mem := (
        0  => "0010100110010101",
        1  => "1000001100111001",
        2  => "11111100000000101",
        3  => "0010000001001001",
        4  => "0000000110000000",
        5  => "1000000000000011",
        6  => "1010000000101001",
        7  => "XXXXXXXXXXXXXXXX");
begin
    process (address)
    begin
        if (RD = '1') then
            case address is
                when "000000" => data <= my_rom(0);
                when "000001" => data <= my_rom(1);
                when "000010" => data <= my_rom(2);
            end case;
        end if;
    end process;
end architecture behavioral of memory;

```



```

        when "000011" => data <= my_rom(3);
        when "000100" => data <= my_rom(4);
        when "000101" => data <= my_rom(5);
            when "000110" => data <= my_rom(6);
            when "000111" => data <= my_rom(7);
        when others => data <= "0000000000000000";
    end case;
end if;
end process;
end architecture behavioral;

```

datapath.vhd:

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;

--Control Word ranges
-- Range DA(15:13)
-- Range AA(12:10)
-- Range BA(9:7)
-- Range MB(6)
-- Range FS(5:2)
-- Range MD(1)
-- Range RW(0)

entity datapath is
port(
    CONTROL_WORD: in std_logic_vector(15 downto 0);
    V, C, N, Z: out std_logic;
    CLK: in std_logic;
    Constant_in : in std_logic_vector(7 downto 0);
    DATA_in: in std_logic_vector(7 downto 0);
    DATA_out: out std_logic_vector(7 downto 0)
);
end entity;

architecture BEHAVIORAL of datapath is

    signal FS : std_logic_vector(3 downto 0);
    signal DA : std_logic_vector(2 downto 0);
    signal AA : std_logic_vector(2 downto 0);
    signal BA : std_logic_vector(2 downto 0);
    signal MB, MD, RW : std_logic;

    signal A, B_mux, B, D_mux, D: std_logic_vector(7 downto 0);

    component reg_file
        port(
            DA, AA, BA: in std_logic_vector(2 downto 0);

```

```

        RW: in std_logic;
        CLK: in std_logic;
        DATA: in std_logic_vector(7 downto 0);
        A_data, B_data: out std_logic_vector(7 downto 0)
    );
end component;

component fun_file
port(
    FS: in std_logic_vector(3 downto 0); -- Function Select
    V, C, N, Z: out std_logic;           -- Signal Out
    AF_data, BF_data: in std_logic_vector(7 downto 0); -- Function unit data
input
    DF_data: out std_logic_vector(7 downto 0) -- Function unit data output
);
end component;

begin

    DA <= CONTROL_WORD(15 downto 13);
    AA <= CONTROL_WORD(12 downto 10);
    BA <= CONTROL_WORD(9 downto 7);
    MB <= CONTROL_WORD(6);
    FS <= CONTROL_WORD(5 downto 2);
    MD <= CONTROL_WORD(1);
    RW <= CONTROL_WORD(0);

    process(MB,B)
    begin
        case MB is
            when '1' => B_mux <= Constant_in;
            when others => B_mux <= B;
        end case;
    end process;

    func_unit: fun_file port map (FS => FS, V => V, C => C, N => N, Z => Z, AF_data =>
    A, BF_data => B_mux, DF_data => D);

    reg_unit: reg_file port map (DA => DA, AA => AA, BA => BA, RW => RW, CLK => CLK,
    DATA => D_mux, A_data => A, B_data => B);

    process(MD,D)
    begin
        case MD is
            when '1' => D_mux <= DATA_in;
            when others => D_mux <= D;
        end case;
    end process;

    process(RW)
    begin

```

```

        if (RW = '0') then
            DATA_OUT <= B_MUX;
        else
            DATA_OUT <= "00000000";
        end if;
    end process;
end architecture BEHAVIORAL;

```

reg_file.vhd:

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;

entity reg_file is
port(
    DA, AA, BA: in std_logic_vector(2 downto 0);
    RW: in std_logic;
    CLK: in std_logic;
    DATA: in std_logic_vector(7 downto 0);
    A_data, B_data: out std_logic_vector(7 downto 0)
);
end entity;

architecture BEHAVIORAL of reg_file is
    signal R0 : std_logic_vector(7 downto 0) := B"00000000";
    signal R1 : std_logic_vector(7 downto 0) := B"00000001";
    signal R2 : std_logic_vector(7 downto 0) := B"00000010";
    signal R3 : std_logic_vector(7 downto 0) := B"00000011";
    signal R4 : std_logic_vector(7 downto 0) := B"00000100";
    signal R5 : std_logic_vector(7 downto 0) := B"00000101";
    signal R6 : std_logic_vector(7 downto 0) := B"00000110";
    signal R7 : std_logic_vector(7 downto 0) := B"00000111";

begin

    process (AA)
    begin
        case AA is
            when "000" => A_data <= R0;
            when "001" => A_data <= R1;
            when "010" => A_data <= R2;
            when "011" => A_data <= R3;
            when "100" => A_data <= R4;
            when "101" => A_data <= R5;
            when "110" => A_data <= R6;
            when others => A_data <= R7;
        end case;
    end process;
end process;

```

```

process (BA)
begin
    case BA is
        when "000" => B_data <= R0;
        when "001" => B_data <= R1;
        when "010" => B_data <= R2;
        when "011" => B_data <= R3;
        when "100" => B_data <= R4;
        when "101" => B_data <= R5;
        when "110" => B_data <= R6;
        when others => B_data <= R7;
    end case;
end process;

process (DA, CLK)
begin
    if (rising_edge(CLK) and RW = '1') then
        case DA is
            when "000" => R0 <= DATA;
            when "001" => R1 <= DATA;
            when "010" => R2 <= DATA;
            when "011" => R3 <= DATA;
            when "100" => R4 <= DATA;
            when "101" => R5 <= DATA;
            when "110" => R6 <= DATA;
            when others => R7 <= DATA;
        end case;
    end if;
end process;
end architecture BEHAVIORAL;

```

fun_file.vhd:

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.numeric_std.all;
use ieee.std_logic_unsigned.all;

-- FS is the function select of the arithmetic operation.
-- V, C, N, Z are the signal output for the ALU to control unit.
entity fun_file is
port(
    FS: in std_logic_vector(3 downto 0); -- Function Select
    V, C, N, Z: out std_logic;           -- Signal Out
    AF_data, BF_data: in std_logic_vector(7 downto 0); -- Function unit data
input

```

```

        DF_data: out std_logic_Vector(7 downto 0) -- Function unit data output
    );
end entity;

architecture BEHAVIORAL of fun_file is
begin

    process (FS, BF_data, AF_data)
    begin
        case FS is
            when "0000" => DF_data <= AF_data;
            when "0001" => DF_data <= AF_data + 1;
            when "0010" => DF_data <= AF_data + BF_data;
            when "0011" => DF_data <= AF_data + BF_data + 1;
            when "0100" => DF_data <= AF_data + not(BF_data);
            when "0101" => DF_data <= AF_data + not(BF_data) + 1;
            when "0110" => DF_data <= AF_data - 1;
            when "0111" => DF_data <= AF_data;
            when "1000" => DF_data <= AF_data and BF_data;
            when "1001" => DF_data <= AF_data or BF_data;
            when "1010" => DF_data <= AF_data xor BF_data;
            when "1011" => DF_data <= not(AF_data);
            when "1100" => DF_data <= BF_data;
            when "1101" => DF_data <= '0' & BF_data(7 downto 1);
            when "1110" => DF_data <= BF_data(6 downto 0) & '0';
            when others => DF_data <= B"00000000";
        end case;
    end process;

end architecture BEHAVIORAL;

```